


The background of the image is a dark blue field filled with a complex, glowing circuit board pattern. The circuit lines are light blue and white, forming a dense network of paths, loops, and junctions. Various electronic symbols, such as small squares, rectangles, and clusters of dots, are scattered throughout the circuitry, adding to the technical aesthetic.

Circuits Workshop

By Dallas and Daniel


What Are Circuits?

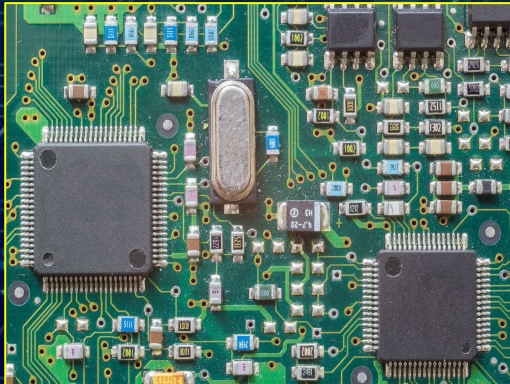- A circuit is a continuous path through which electricity flows.
- It starts at a power source, such as a battery, travels through a load to perform a specific task, and then returns to the source.
- Circuits are essential to many devices and systems that power and support our daily lives.



What Will We Be Making?

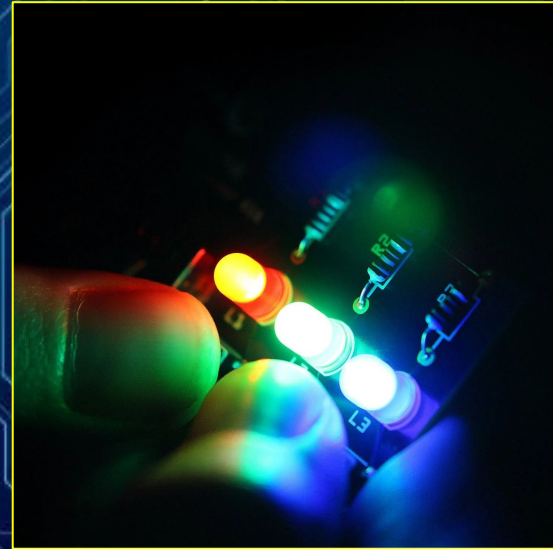- We will be soldering a small circuit that allows you to press three buttons - each one lighting up a different LED: blue, green, or red.



Voltage, Current, and Resistance

- Voltage is the difference in electric potential energy per unit charge.
 - The unit for voltage is the volt, symbolized as V.
- Current represents the flow of electrons and indicates the rate at which they move.
 - The unit for current is the ampere (amp), symbolized as I.
 - Think of it like water flow: if the water flows quickly, the current is higher; if it flows slowly, the current is lower.
- Resistors are used to provide resistance.
 - Resistors limit the flow of current.
 - The unit for resistance is the Ohm, symbolized by the Greek letter omega (Ω).
- Use the equation $V = IR$ to calculate voltage. This formula can be rearranged to solve for current or resistance.


Series and Parallel Circuits

- **Series Circuit**

- Electricity flows from one component to the next in a single path.
- As the current passes through each component, the voltage gradually decreases.
- The current is constant across the circuit.

- **Parallel Circuit**

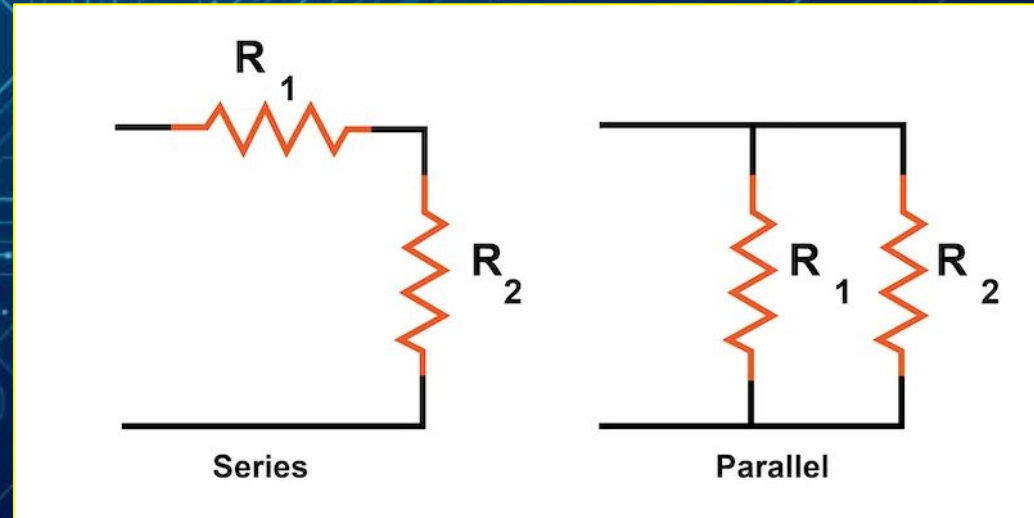- All components are connected across the same two points, so each one receives full voltage from the power source.
- The current is divided among the parallel branches.
- The voltage is constant across the circuit.






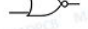



Capacitors

- A capacitor is an electronic component that stores electrical charge.
- It consists of two conductive plates separated by an insulating material called a dielectric.
- When connected to a power source, positive charge accumulates on one plate and negative charge on the other.
- Once the capacitor reaches its capacity and the electrical field is removed, it discharges the stored energy.
- Capacitors are commonly used in sensing, signal processing, energy storage, and motor starters.




Comparators and Gates

- A comparator in a circuit compares two input voltages and determines which is higher. It outputs either a 0 or a 1.
- A logic gate performs a Boolean logic operation on one or more binary inputs and produces a single binary output.
- There are seven types of basic logic gates, shown in the diagram on the right, but we will focus on three today: AND, OR, and NOT.
- The AND gate outputs 1 only if both inputs are 1.
 - For example, if both inputs are 1, the output will be 1.
 - If one input is 0 and the other is 1, the output will be 0.
- The OR gate outputs 1 if one or both inputs are 1.
 - If both inputs are 0, the output will be 0.
- The NOT gate, which is an inverter, reverses the input.
 - If the input is 1, the output will be 0.
 - If the input is 0, the output will be 1.

Logic Gate (AND, OR, XOR, NOT, NAND, NOR & XNOR)			
Logic Gate	Symbol	Description	Boolean
AND		Output is at logic 1 when, and only when all its inputs are at logic 1, otherwise the output is at logic 0.	$X = A \cdot B$
OR		Output is at logic 1 when one or more are at logic 1. If all inputs are at logic 0, output is at logic 0.	$X = A + B$
NAND		Output is at logic 0 when, and only when all its inputs are at logic 1, otherwise the output is at logic 1.	$X = \overline{A \cdot B}$
NOR		Output is at logic 0 when one or more of its inputs are at logic 1. If all the inputs are at logic 0, the output is at logic 1.	$X = \overline{A + B}$
XOR		Output is at logic 1 when one and only one of its inputs is at logic 1. Otherwise it is logic 0.	$X = A \oplus B$
XNOR		Output is at logic 0 when one and only one of its inputs is at logic 1. Otherwise it is logic 1. Similar to XOR but inverted.	$X = \overline{A \oplus B}$
NOT		Output is at logic 0 when its only input is at logic 1, and at logic 1 when its only input is at logic 0. That's why it is called AND INVERTER.	$X = \overline{A}$

What Is Soldering?

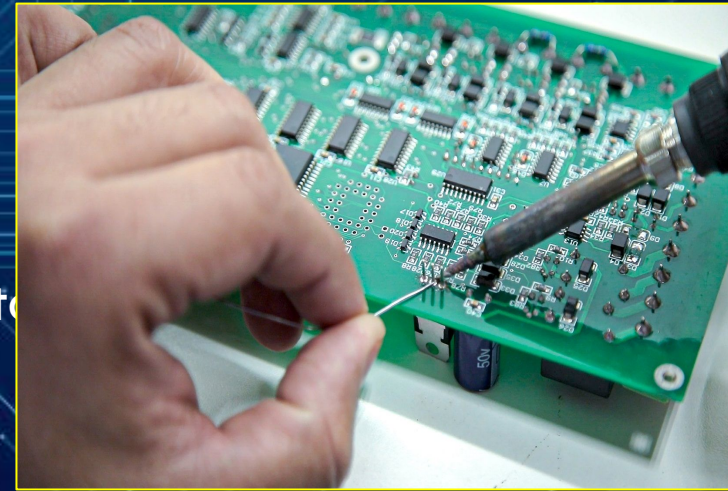- Soldering is the process of joining two or more metal components together by melting a filler metal called solder.
- Soldering requires a few key tools: a soldering iron to heat the solder, solder wire as the bonding material, a soldering stand to safely hold the hot iron, and flux to clean the tip of the iron.



Soldering Tutorial





Thanks for Attending!

We hope you enjoy the remainder of HackBI IX!